

Section 1: Simple OPS Analysis

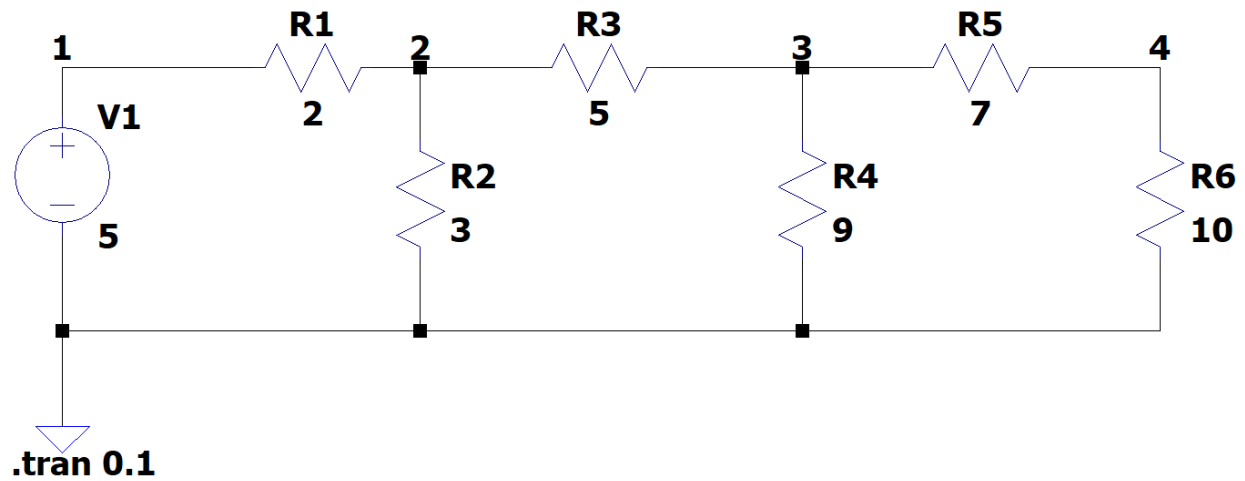


Figure 1: IRV circuit that was analyzed using OPS analysis in Python from LTspice



Figure 2: Timing diagram of the IRV circuit that was analyzed with OPS in Python from LTspice

```
OP simulation results for 'Simple Example Circuit'.
Run on 2022-10-01 15:35:10, data file C:\Users\pskon\AppData\Local\Temp\tmprdgc_pgf.op.
```

Variable	Units	Value	Error	%
VN1	V	5	-5.00022e-12	0
VN2	V	2.7021	-2.70228e-12	0
VN3	V	1.46085	-1.46083e-12	0
VN4	V	0.859325	-8.59313e-13	0
I(V1)	A	-1.14895	0	0

Figure 3: Output for the OPS analysis of the IRV circuit from figure 1

The voltage measurements at node 1, 2, 3, and 4 from figure 3 match the gain/voltage measurements values visually at the same nodes in LTspice in figure 2; OPS analysis provides greater precision with decimal place values going up to one hundred thousandths. So, both methods can be used for simple circuit design and analysis.

Section 2: Simple AC and Trans Analysis

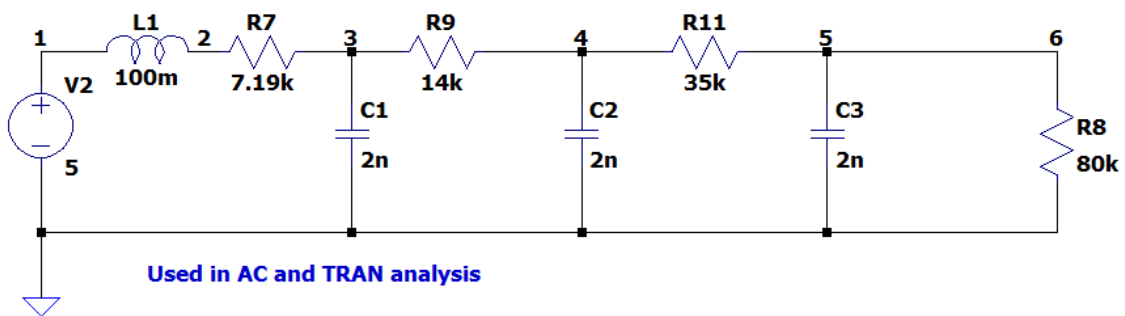


Figure 4: RCL circuit used in AC and TRAN analysis

Section 3: Simple PZ (Pole-Zero) analysis

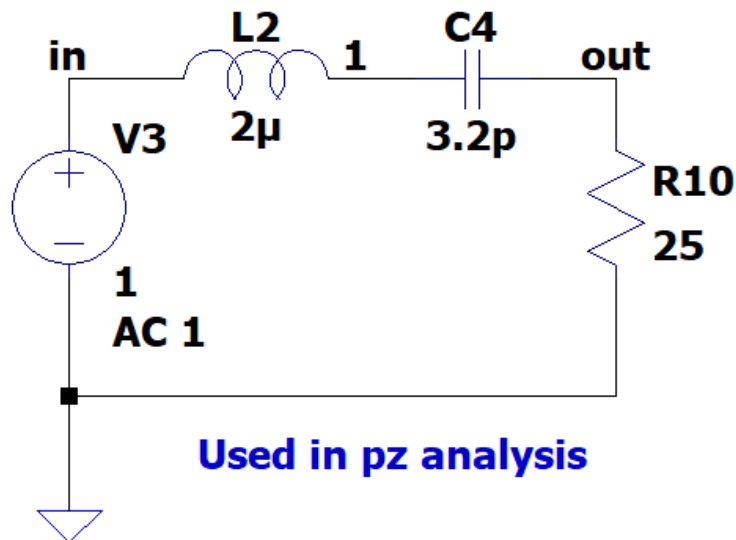


Figure 5: RCL circuit used in pz analysis